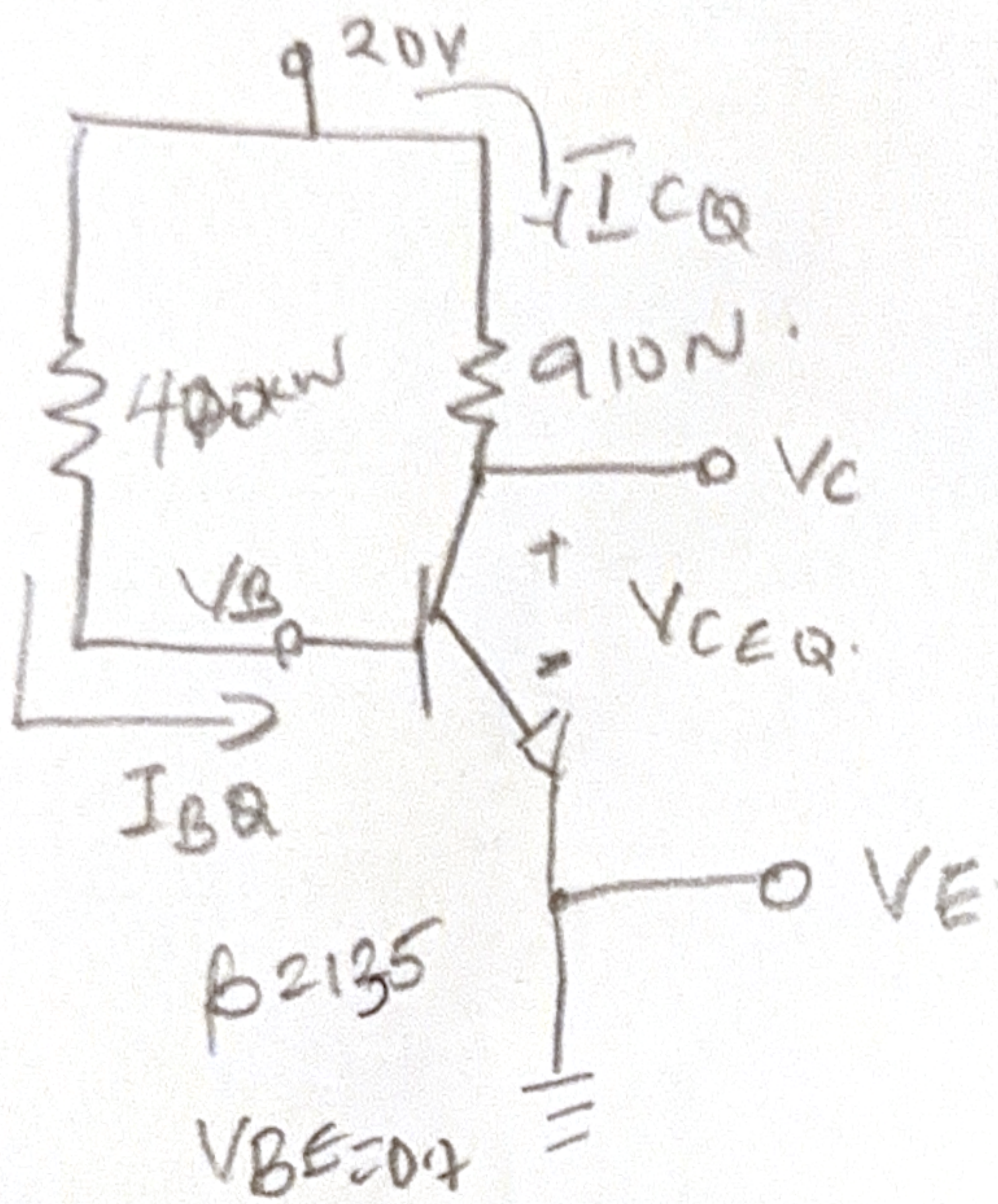




$$I_C = \beta I_B$$

$$I_E = I_C + I_B$$

$$I_E = (\beta + 1) I_B$$

$$I_E = I_C$$

$$V_{CC} = 20V$$

$$R_B = 470k\Omega$$

$$R_C = 910\Omega$$

$$\beta = 135$$

$$V_{BE} = 0.7V$$

Emitter is grounded = 0

$$(1) I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_B = \frac{20 - 0.7}{470000} = \frac{19.3}{470000}$$

$$= 4.106 \times 10^{-5} A$$

$$I_B = 41 \mu A$$

$$(2) I_C = \beta I_B$$

$$I_C = 135 \times 41 \mu A$$

$$I_C = 5.54 mA$$

$$(3) I_E = I_C + I_B$$

$$I_E = 5.54 + 0.041 mA$$

$$I_E = 5.58 mA$$

$$(4) V_C$$

$$V_{RC} = I_C R_C$$

$$V_{RC} = 5.54 mA \times 910\Omega = 5.04 V$$

$$V_C = V_{CC} - V_{RC}$$

$$V_C = 20 - 5.04 = 14.96 V$$

$$V_B = V_B = V_{BE} = 0.74.$$

$$b) V_E = V_E = 0.4$$

$$V_{CE} = V_C - V_E$$

$$V_{CE} = 14.96 - 0 \\ = 14.964 \\ =$$

$$Q_{point} = (V_{CE} = 15.4, I_C = 5.5mA)$$